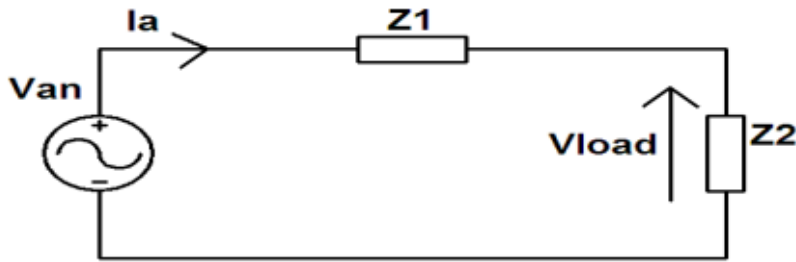


Using Smath for Electrical Engineering (Complex Domain with units)

Example created by Smath forum user kevnol 17 June 2013

**Parameters**

$$V_{an} := 230 \text{ V}$$

$$Z1 := (1 + i \cdot 2) \Omega \quad Z2 := (10 + i \cdot 5) \Omega$$

Calculating the Current

$$I_a := \frac{V_{an}}{Z1 + Z2} \quad I_a = (14.88 - 9.47 \cdot i) \text{ A}$$

$$\text{Polar Form} \quad |I_a| = 17.64 \text{ A} \quad \arg\left(\frac{I_a}{1 \text{ A}}\right) = -32.47^\circ$$

Note: Current version of Smath (0.96 build 4909) cannot take $\arg()$ of a number with units. Dividing by 1 Amp removes the units to allow $\arg()$ to be used

Load Voltage

$$V_{load} := I_a \cdot Z2 \quad V_{load} = (196.18 - 20.29 \cdot i) \text{ V}$$

$$\text{Polar Form} \quad |V_{load}| = 197.22 \text{ V} \quad \arg\left(\frac{V_{load}}{1 \text{ V}}\right) = -5.91^\circ$$

Complex Power

$$S_{load} := V_{load} \cdot \text{conj}(I_a) \quad S_{load} = 3111.76 + 1555.88 \cdot i \text{ VA}$$

$$P := \text{Re}\left(\frac{S_{load}}{1 \text{ VA}}\right) \text{ W} \quad P = 3111.76 \text{ W}$$

$$Q := \text{Im}\left(\frac{S_{load}}{1 \text{ VA}}\right) \text{ var} \quad Q = 1555.88 \text{ var}$$

$$\text{PF} := \frac{P}{|S_{load}|} \quad \text{PF} = 0.89$$

Custom Units

$$VA := W$$

$$\text{var} := W$$

Note: VA and var are dimensionally equivalent to Watts but Elec Eng uses them for apparent and reactive power

Custom Function

$$\text{conj}(x) := \frac{|x|^2}{x}$$

Note: Complex Conjugate function Useful for calculating Complex Power

Note: Magnitude function is entered as $\text{abs}()$